
ECE 376 - Homework #1

PIC Background. Due Wednesday, January 18th

Please submit in class or online as a Word /pdf file submitted via BlackBoard or email with header ECE 376 HW1

Please submit in class of online as a word /pdf file submitted via BlackBoard of email with neader EC	JL 37011VV1	
Problem	Answer	
1) A PIC's output is limited to 25mA. Assuming V2 is 5V, what is the smallest resistance you can connect to the output? (How small can R3 be?) $R = \frac{5}{25 \cdot 10^{-3}} = 200 \Omega$	$R3 = 200 \Omega$	
A PIC can measure voltage to 4.88mV. To give an idea of how small this is		
2) What is the smallest change in R2 a PIC can measure if R2 = 800 Ohms nominally?		
• How much does R2 have to change from 800 Ohms for V1 to change by 4.88mV?		
$V_1 = \frac{R_2}{R_2 + R_1} \cdot V_{IN} = \frac{800}{800 + 1000} \cdot 5 = \frac{20}{9} V \approx 2.22 V$	$R = 3.1678\Omega$	
$V_1 = \frac{20}{9} + 4.88 \cdot 10^{-3} = 2.2271 V$ 2.2271		
$R_2 = \frac{2.2271}{5-2.2271} \cdot 1000 = 803.1678 \Omega$ The smallest change in resistance a PIC can see is $R=803.1678-800=3.1678 \Omega$		
3) Assume R2 is a thermistor. • What temperature is it if R2 = 800 Ohms? $R_2 = 1000 \cdot \exp\left(\frac{3905}{T + 273} - \frac{3905}{298}\right) \Omega$ $R_2 = 800 \ \Omega \rightarrow T = 30.1624 \ ^{\circ}C$ • How much does the temperature have to change for V1 to change by 4.88mV? $R_2 = 803.1678 \ \Omega \rightarrow T = 30.0695 \ ^{\circ}C$ The smallest change in temperature a PIC can detect is $T = 0.0929 \ ^{\circ}C$	$T = 0.0929 ^{\circ}C$	
A PIC can measure time to 100ns. To give an idea of how small this is		
4) The fastest hockey puck shot was 110.3 mph (46.98 m/s) by Denis Kulyash in 2011. If the puck travels 89 feet to the net (shot from mid-line),		
• How long does it take to travel to the net? $d = v \cdot t$ $27.1272 = 46.98 \cdot t$ $t = 0.5774201788 s$	$t = 0.5774201788 s$ $\Delta v = 0.00000813618 \frac{m}{s}$	
 How much faster would the puck have to travel for it to take 100ns less to travel this distance? 	s. s.sssssssssssssssssssssssssssssssss	
$v = \frac{t = 0.5774202788 s}{27.1272} = 46.97999186 \frac{m}{s}$		


5) The world record for a 500m speed skate is 38.9 seconds (Hasse Borjes in 1970). How far behind would you have to be (in meters) if you cross the finish line 100ns behind Hasse Borjes? $d = \frac{500}{38.9} \cdot 100 \cdot 10^{-9} = 0.00000128534 m$ $d = 1.28534 \mu m$	$d = 1.28534 \mu m$
6) Assume for the 555 timer • R1 = 1k, R2 = 800, C = 0.22uF • What frequency does the 555 timer output on pin #3? $T = (R_1 + 2R_2) \cdot C \cdot \ln(2)$ $T = (1k + 2 \cdot 800) \cdot 0.22\mu \cdot \ln(2) = 0.39648 ms$ $f = \frac{1}{T} = 2522.19 Hz$	f = 2522.19 Hz
7) What is the smallest change in frequency a PIC can detect? • i.e. how much does the frequency have to change for the period to change by 100ns? $T = 0.39648ms + 100ns = 0.39658 ms$ $f = \frac{1}{T} = 2521.56 Hz$ $\delta f = 0.63 Hz$	$\delta f = 0.63 Hz$
8) With this circuit, you can build an Ohm-meter (replace R2 with the resistance to be measured.) Assume R2 = 800 Ohms (nominally). How much does R2 have to change for the period to change by 100ns? • i.e. What is the resolution of this circuit when used as an Ohm-meter? $T = 0.39658 \ ms = (1k + 2 \cdot R_2) \cdot 0.22 \mu \cdot \ln(2)$ $R_2 = 800.3273 \ \Omega$ A PIC can detect a change in resistance of $R = 0.3273 \ \Omega$	$R=0.3273\Omega$
9) Replace R2 with a thermistor. How much does the temperature have to change for the period to increase by 100ns ? • i.e. what is the resolution in degrees C? $R_2 = 1000 \cdot \exp\left(\frac{3905}{T + 273} - \frac{3905}{298}\right) \Omega$ $R_2 = 800 \ \Omega \rightarrow T = 30.1624 \ ^{\circ}C$ $R_2 = 800.3273 \ \Omega \rightarrow T = 30.1528 \ ^{\circ}$ The smallest change in temperature a PIC can detect is $T = 0.0096 \ ^{\circ}C$	T = 0.0096 °C

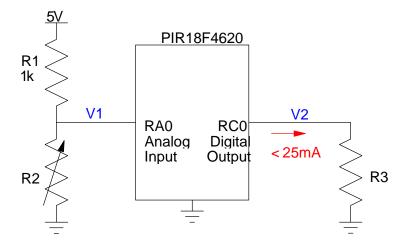

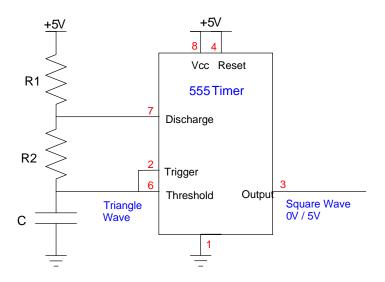Problem #1 to #3

If R2 is a thermistor, assume

$$R_2 = 1000 \cdot \exp\left(\frac{3905}{T + 273} - \frac{3905}{298}\right) \Omega$$



Astable 555 Timer: Problems 5-8 The square wave at the Output has a period of $T=(R_1+2R_2)\cdot\mathcal{C}\cdot\ln(2)$ seconds